

# Sequence Logic and ALU


## Memory

Implementation of memory elements involves synchronization, clocking and feedback loops
 
## Clock

The hardware implementation is based on an **oscillator** that alternates between the beginning phases labelled:



The elapsed time between the beginning of a tick and the end of a subsequent tock is called a **cycle**


 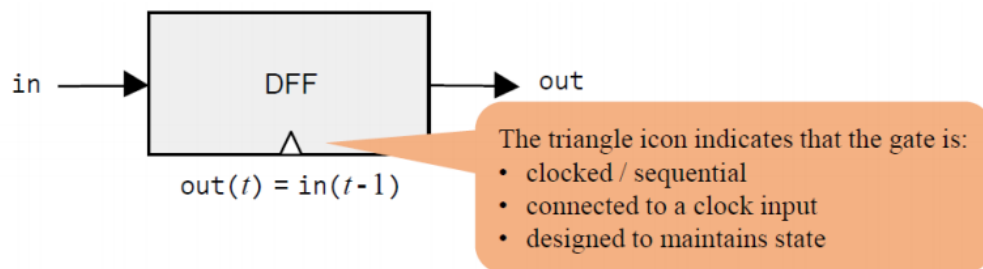
## Flip Flops

**Data Flip Flop (DFF):** the simplest **state keeping** gate (built-in)

The gate outputs its previous input:  $out(t) = in(t-1)$



## Data and Time in DFF

$out(t) = in(t-1)$

- **in** is the gate's input value
- **out** is the gate's output value
- **t** is the current clock cycle
- **t-1** is the previous clock cycle
- **t+1** is the next clock cycle

This elementary behavior can form the basis of all the hardware devices that computers use to maintain state

## Sequential Chips


Sequential chips are capable of:

- Maintaining state
- Acting on the state, and on the current inputs

$$state(t) = f(state(t-1), input(t))$$

## Sequential Chips


- Calculate -> Save

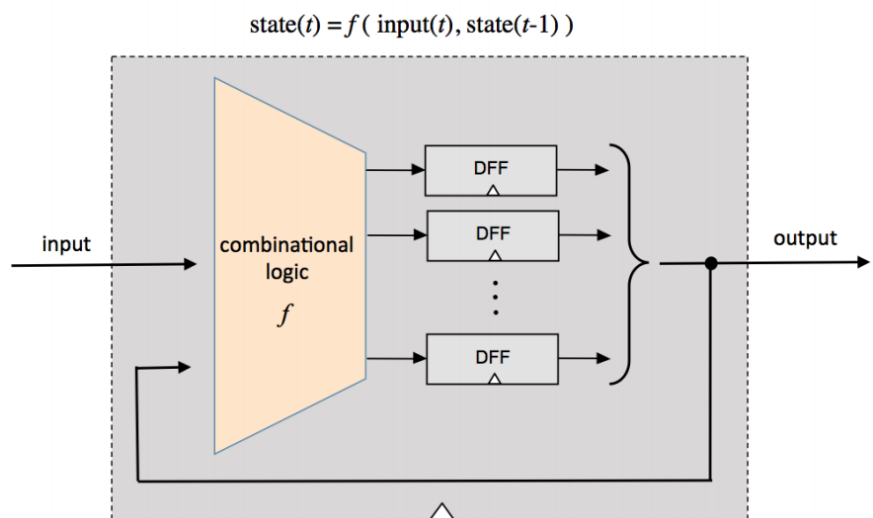


## Register

A register is a storage device that can **“store”** or **“remember”** a value over time


### 1-bit register

 

 if  $\text{load}(t)$  then  $\text{out}(t+1) = \text{in}(t)$   
 else  $\text{out}(t+1) = \text{out}(t)$




### 1-bit Register: Implementation

 
 
# Memory Hierarchy

As it goes further, capacity and latency increase



## Random-Access Memory (RAM)


RAM should be able to access randomly chosen words, with no restriction in the order in which they are accessed

**only maintains its data while the device is powered**

Random-Access Memory has:

- A data input
- An address input
- A load bit (read is load=0, write is load=1)


## Multi-bit Registers

 

if load(t-1) then out(t)=in(t-1)  
else out(t)=out(t-1)


*w-bit register*

## The IAS (von Neumann) Machine

 

 
## Arithmetic Logical Unit

- A **combinational circuit** that performs arithmetic and bitwise operations on integers represented as binary numbers.
- Input the **data** and some **code for the operation**
- Output will be some **data** and any **additional information**


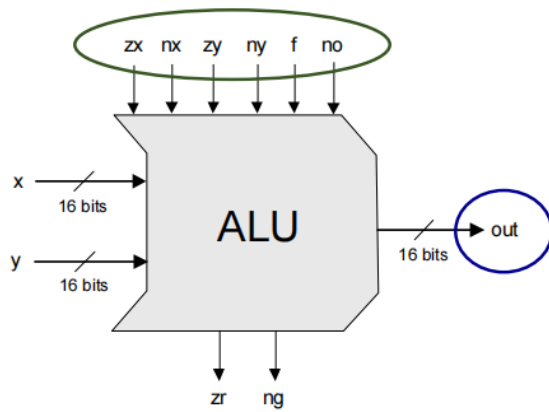
# The Hack ALU

To cause the ALU to compute a function, set the control bits to one of the binary combinations listed in the table.



control bits						
zx	nx	zy	ny	f	no	out
1	0	1	0	1	0	0
1	1	1	1	1	1	1
1	1	1	0	1	0	-1
0	0	1	1	0	0	x
1	1	0	0	0	0	y
0	0	1	1	0	1	!x
1	1	0	0	0	1	!y
0	0	1	1	1	1	-x
1	1	0	0	1	1	-y
0	1	1	1	1	1	x+1
1	1	0	1	1	1	y+1
0	0	1	1	1	0	x-1
1	1	0	0	1	0	y-1
0	0	0	0	1	0	x+y
0	1	0	0	1	1	x-y
0	0	0	1	1	1	y-x
0	0	0	0	0	0	x&y
0	1	0	1	0	1	x y